

Please read carefully before starting:

- Simulation tool to be used is National Instruments (NI) Multisim.
- The setup of the NMOS and PMOS transistors and their models are given at the end of the document.
- You should be divided into groups of three students.
- Each group should be ready for a discussion in the project (schematics and simulations results on Multisim are needed).
- You are required to deliver a hard copy report that contains:
 1. Schematic diagrams (snapshots from Multisim showing dimensions and values)
 2. Design procedure (hand calculations)
 3. Simulation results (snapshots from Multisim)
 4. Discussion of your results and conclusions

Any missing item from the 4 items above will be penalized in the report grading.

- The total grade of the project is 15 points.
- The deadline to submit the project report (delivered to the classroom) April 24th, 2020.
- Any copied will be given zero.

1. Transistor Characterization:

 


Fig. 1 Transistor Characterization

(a) For the schematic shown in Fig. 1 with $W=10\mu\text{m}$, $L=1\mu\text{m}$:

- Perform DC sweep for V_{out} (from 0 to 3V) while $V_{in}=2\text{V}$ and plot I_D vs. V_{out} .
- Perform DC sweep for V_{in} (from 0 to 3V) while $V_{out}=2\text{V}$ and plot I_D vs. V_{in} .
- From the above curves determine the value of V_{TH} , $\mu_n C_{OX}$, and λ .
- Repeat the above for $W=20\mu\text{m}$, $L=2\mu\text{m}$.
- Discuss your results

(b) Repeat (a) for a PMOS device with the same dimensions.

(c) Compare between NMOS and PMOS devices.

(d) Discuss your results

2. Current mirrors:

Compliance voltage is the minimum voltage V_{out} for the circuit to operate as a current mirror.

 


Fig 2(a) Simple Current Mirror

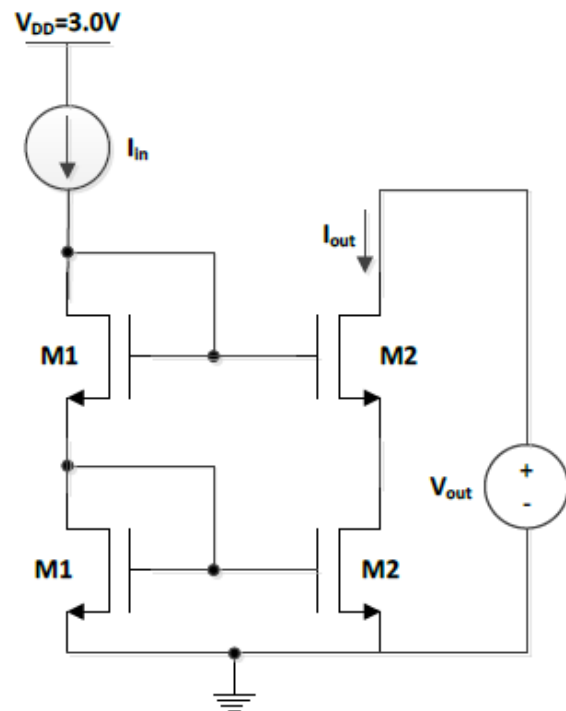


Fig 2(b) Cascode Current Mirror

(a) Design the simple current mirror in Fig. 2(a) such that $I_{in}=100\mu A$, $I_{out}=200\mu A$, and V_{eff} is 0.25V for all transistors. $L=1\mu m$.

- Calculate the compliance voltage.
- Perform a DC sweep for V_{out} (from 0 to 3V) and plot I_{out} vs. V_{out} . Plot the percentage error in the output current (relative to the ideal value). Report the compliance voltage from those simulations and compare with calculations.
- Choose a proper DC value of V_{out} (more than the compliance voltage), run AC analysis to plot R_{out} vs frequency (up to 10GHz).

Repeat (a) for $I_{in}=200\mu A$ and $I_{out}=400\mu A$. V_{eff} should be kept at 0.25V.

(b) Use the same design from Fig. 2(a) to construct the cascode current mirror in Fig. 2(b). Repeat the same simulations.

3. Differential Pairs:


 


Fig. 4 Differential Amplifier

 
- (a) Design the differential buffer shown in Fig. 4 with the following specifications:
- $ADM \geq 5$
 - Input linear range $\geq 0.2V$
 - Differential output voltage swing $\geq 1.0V_{pp}$ (peak to peak)
- (b) Calculate the common-mode input range for your design.
- (c) Document the design procedure and the results of the following simulations:
- DC analysis and show the Q-point (I_D , V_{DS} , V_{eff}) of all transistors.
 - DC sweep for V_{id} from $-1.8V$ to $1.8V$ and plot i_{D1} , i_{D2} , and i_{OD} .
 - AC analysis and show the small-signal differential gain ADM , conversion gain $ACM-DM$ (due to for 5% mismatch in the two resistors R), and $CMRR$ vs. frequency.
 - Transient analysis with
 $V_{in1} = DC + A \cdot \sin(2\pi ft) + B \cdot \sin(4\pi ft)$, $V_{in2} = DC - A \cdot \sin(2\pi ft) + B \cdot \sin(4\pi ft)$.
Plot V_{in1} , V_{in2} , V_P , V_{out1} , V_{out2} , V_{outd} . Where $A = 10mV$, $B = 10mV$, $f = 1MHz$, DC is a proper DC value of your choice.
- (d) **Discuss your results.**
- Note:** The differential inputs V_{in1} and V_{in2} can be generated using an ideal transformer or ideal voltage controlled voltage source (VCVS).

Setup of the NMOS and PMOS transistors:

Choose an NMOS_4T from the menu of **Place** → **Component** (as shown below) and place it in your schematic.



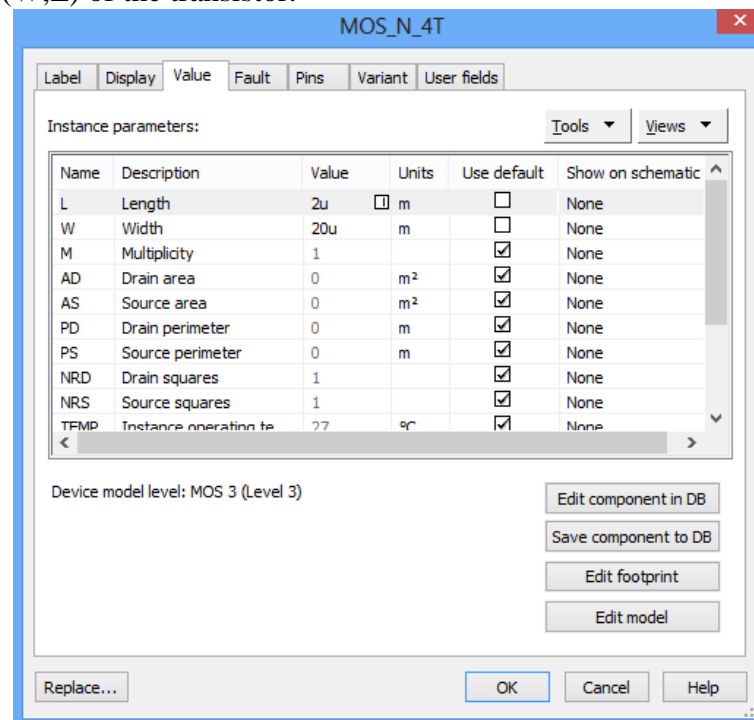
Double click on the transistor and choose the tab of “Value”. This is where you can change the dimensions (W,L) of the transistor.



Click on the “Edit model” button.

Copy and paste the model of the NMOS (as shown) in the “SPICE view”

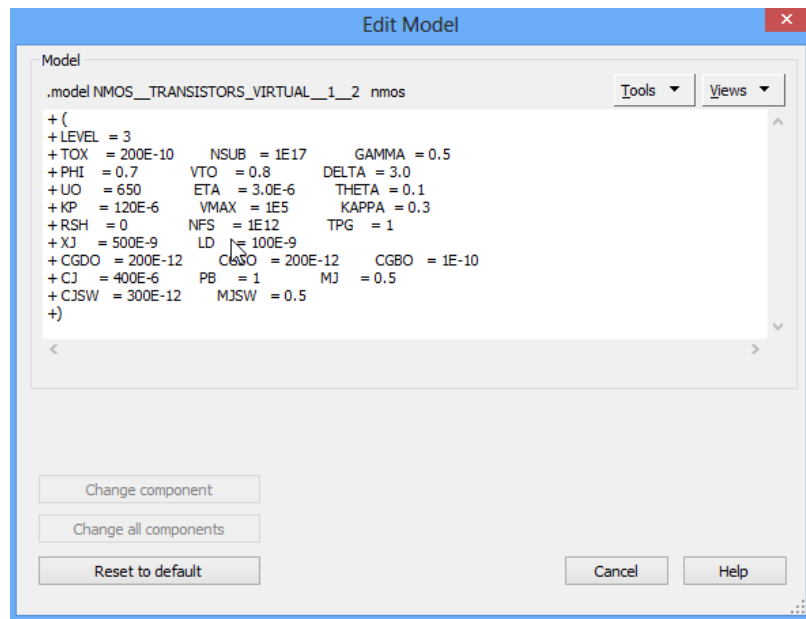Make sure to click on the “Change component” button to save changes.



If you need to place another transistor in a schematic, copy the transistor that you have just created to get the correct model and you can then change the dimensions.

Repeat the same for the PMOS transistor (MOS_P_4T).

Minimum length of any transistor is $1\mu\text{m}$. The bulk of an NMOS device should be connected to lowest voltage (ground) and that of a PMOS device should be connected to the highest voltage (V_{DD}).

NMOS:

```
+ (
+ LEVEL = 3
+ TOX = 200E-10    NSUB = 1E17    GAMMA = 0.5
+ PHI = 0.7        VTO = 0.8      DELTA = 3.0
+ UO = 650          ETA = 3.0E-6   THETA = 0.1
+ KP = 120E-6       VMAX = 1E5     KAPPA = 0.3
+ RSH = 0           NFS = 1E12     TPG = 1
+ XJ = 500E-9       LD = 100E-9
+ CGDO = 200E-12    CGSO = 200E-12    CGBO = 1E-10
+ CJ = 400E-6       PB = 1         MJ = 0.5
+ CJSW = 300E-12    MJSW = 0.5
+ )
```

PMOS:

```
+ (
+ LEVEL = 3
+ TOX = 200E-10    NSUB = 1E17    GAMMA = 0.6
+ PHI = 0.7        VTO = -0.9     DELTA = 0.1
+ UO = 250          ETA = 0         THETA = 0.1
+ KP = 40E-6        VMAX = 5E4     KAPPA = 1
+ RSH = 0           NFS = 1E12     TPG = -1
+ XJ = 500E-9       LD = 100E-9
+ CGDO = 200E-12    CGSO = 200E-12    CGBO = 1E-10
+ CJ = 400E-6       PB = 1         MJ = 0.5
+ CJSW = 300E-12    MJSW = 0.5
+ )
```